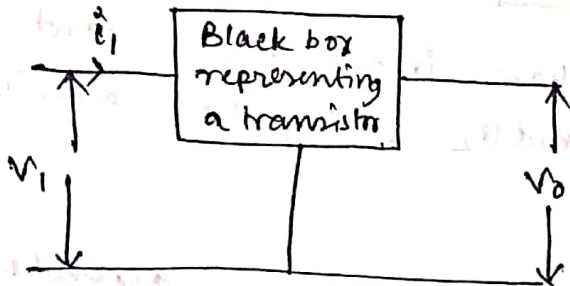


Two port analysis of a transistor

Transistor - two port or four terminal network

↳ two voltages, + two currents



i_1, v_o - independent variable

v_i, i_o - dependent variable

$$v_i = f_1(i_1, v_o) \quad \text{--- (1)}$$

$$i_o = f_2(i_1, v_o) \quad \text{--- (2)}$$

i_1, i_o, v_i, v_o represent total instantaneous values consisting of d.c. and a.c. parts.

Let $i_1 = I_1 + i_1$ capitals - d.c. part.

$i_o = I_o + i_o$ small - a.c. part.

$v_i = V_i + v_i$ Assume a.c. part \ll d.c. part.

$v_o = V_o + v_o$

Taylor's series expansion of (1) and (2) about the d.c. operating point and neglecting higher order terms.

$$v_i = \left. \frac{\partial v_i}{\partial i_1} \right|_{v_o} \cdot i_1 + \left. \frac{\partial v_i}{\partial v_o} \right|_{i_1} \cdot v_o$$


$$i_o = \left. \frac{\partial i_o}{\partial i_1} \right|_{v_o} \cdot i_1 + \left. \frac{\partial i_o}{\partial v_o} \right|_{i_1} \cdot v_o$$

As the transistor is assumed to behave linearly over the small region of operation, the partial derivatives becomes const.

$$v_i = h_i i_1 + h_r v_o$$

$$i_o = h_f i_1 + h_o v_o$$

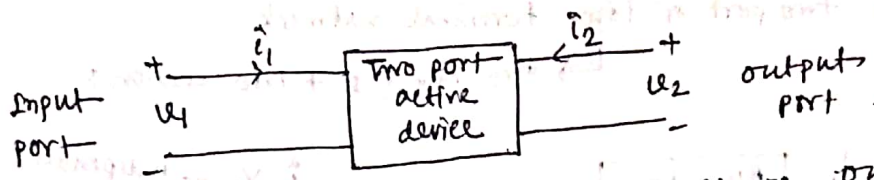Two port devices and different models of a transistor



A two port network is shown in the figure. out of the four quantities i_1, V_1, i_2 and V_2 , any two are independent while two are dependent.

	Independent	dependent
1.	i_1, V_1 (not possible) i_2, V_2	i_2, V_2 i_1, V_1
2.	i_1, V_2 (h-parameter) i_2, V_1	i_2, V_1 i_1, V_2
3.	V_1, V_2 (Y-parameter) i_1, i_2 (Z-parameter)	i_1, i_2 V_1, V_2

The table gives the lists of all possibilities of dependent and independent variables.

1. This possibility is practically not possible. As both i_1, V_1 and i_2, V_2 cannot be independent. (i_1, V_1) and (i_2, V_2) are interrelated according to ohm's law.

Network modelling

1. Z (impedance) parameter model
2. Y (admittance) " "
3. h (hybrid) " "

1. Z parameter model. (i_1, i_2 independent)

We assume that the device is linear.

$$V_1 = Z_{11} i_1 + Z_{12} i_2$$

$$V_2 = Z_{21} i_1 + Z_{22} i_2$$

$$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix} \equiv V = ZI$$

$$Z_{11} = \frac{V_1}{i_1} \Big|_{i_2 = 0}$$


$$Z_{12} = \frac{V_1}{i_2} \Big|_{i_1 = 0}$$

Input impedance when output is open

Reverse transfer impedance when input is open

$$Z_{21} = \left. \frac{u_2}{\hat{i}_1} \right|_{\hat{i}_2=0} \quad \text{forward transfer impedance when output is open}$$

$$Z_{22} = \left. \frac{u_2}{\hat{i}_2} \right|_{\hat{i}_1=0} \quad \text{output impedance when input is open.}$$

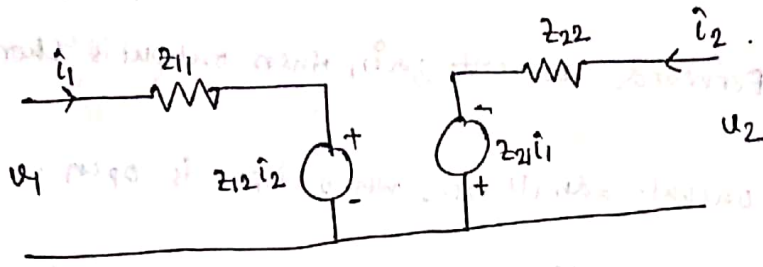

Equivalent circuit.

2. Y parameter model, (u_1, u_2 independent)

$$\hat{i}_1 = Y_{11} u_1 + Y_{12} u_2$$

$$\hat{i}_2 = Y_{21} u_1 + Y_{22} u_2$$

$$\begin{pmatrix} \hat{i}_1 \\ \hat{i}_2 \end{pmatrix} = \begin{pmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{pmatrix} \begin{pmatrix} u_1 \\ u_2 \end{pmatrix} \equiv \mathbf{I} = \mathbf{Y} \cdot \mathbf{V}$$

$$Y_{11} = \left. \frac{\hat{i}_1}{u_1} \right|_{u_2=0}$$

Input admittance when output is short circuited

$$Y_{12} = \left. \frac{\hat{i}_1}{u_2} \right|_{u_1=0}$$


Reverse transfer admittance when input is short circuited

$$Y_{21} = \left. \frac{\hat{i}_2}{u_1} \right|_{u_2=0}$$

forward transfer admittance when output is short circuited

$$Y_{22} = \left. \frac{\hat{i}_2}{u_2} \right|_{u_1=0}$$

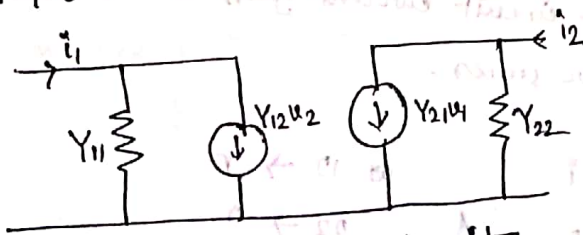output admittance when input is short circuited.



Equivalent circuit.

3. h - (hybrid) parameter model. (u_1, \hat{i}_2 independent, \hat{i}_1, u_2 dependent).

$$u_1 = h_{11} \hat{i}_1 + h_{12} u_2$$

$$\hat{i}_2 = h_{21} \hat{i}_1 + h_{22} u_2$$


$$\begin{pmatrix} u_1 \\ \hat{i}_2 \end{pmatrix} = \begin{pmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{pmatrix} \begin{pmatrix} \hat{i}_1 \\ u_2 \end{pmatrix}$$

$h_{11} = \frac{U_1}{i_1} \Big|_{U_2=0}$ Input impedance when output is short circuited

$h_{12} = \frac{U_1}{U_2} \Big|_{i_1=0}$ Reverse voltage gain when input is open

$h_{21} = \frac{i_2}{i_1} \Big|_{U_2=0}$ Forward current gain when output is short circuited

$h_{22} = \frac{i_2}{U_2} \Big|_{i_1=0}$ Output admittance when input is open

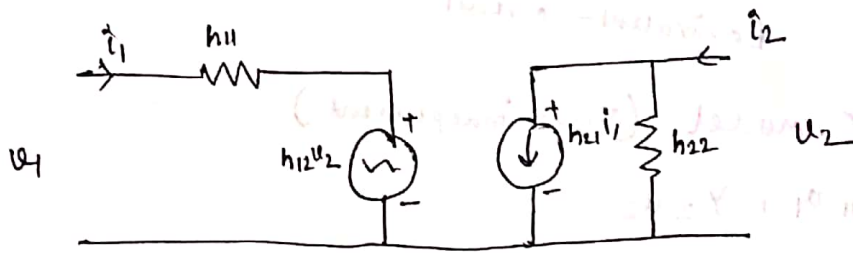

Equivalent circuit:-

This model is called hybrid parameter model because the coefficients (h 's) have different dimensions.

Advantages of h -parameter model

1. h -parameters are easy to measure. They can also be easily determined from the transistor static characteristic curves.
2. h -parameters are real numbers at audio frequencies.
3. Manufacturers usually supply these parameters.
4. h_{fe} represents short circuit current gain. — important quantity in transistor amplifier stages.

Symbols.

$11 \rightarrow i$ $12 \rightarrow r$
 $21 \rightarrow \beta$ $22 \rightarrow 0$

For CE configuration, suffix e is used — $h_{ie}, h_{re}, h_{fe}, h_{oe}$
 For CB and CC, b and c suffix ~~are~~ are used

Are hybrid parameters constant?
 Value of h parameter depend on

- i) position of Q point on the characteristic curve
- ii) temperature of the transistor.